




**What should I already know?**

- Some everyday items that use electricity.
- Sources of sound and light may need electricity to work.
- How to use some tools safely.
- Glue and sticky tape can be used for joining materials.

**What will I know by the end of this unit?**

- Awareness of different battery-powered products.
- Understand designers use a design-make-evaluate process for creating products.
- Mains electricity can be very dangerous.
- To know the components involved in making a simple circuit.
- Tools are essential but need to be used correctly following instructions.
- Designers carry out research to match the product to the individual or group.
- Designers choose the material and components because they best suit the product.
- During the design process constant evaluation against the design brief is needed.

**Handmade switches**

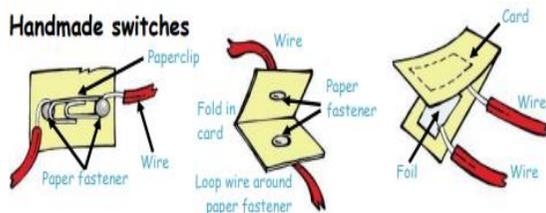

**Design**

- A complete **circuit** is a loop that allows **electrical current** to flow through the **wires**.
- A **circuit** contains a **battery (cell)**, **wires** and an **appliance** that requires **electricity** to work (such as a **bulb**, **motor** or **buzzer**).
- The **electrical current** flows through the **wires** from the **battery (cell)** to the **bulb**, **motor** or **buzzer**.

A **switch** can break or reconnect a **circuit**.

When the **switch** is off, the **electricity** cannot flow. This is not the same as an incomplete **circuit**.



**Design and Technology: Skills and Enquiry**

- Make a variety of **circuits**, investigating which **circuits** work and why.
- Create **circuits** using **switches**.
- Evaluate materials ensuring they are **electrical conductors** and **insulators**.

**Vocabulary**

<b>appliances</b>	An <b>electrical</b> device or machine that you use to do a task such as cleaning or cooking.
<b>battery/cell</b>	Small devices that provide power for <b>electrical</b> items such as torches.
<b>bulbs</b>	The glass part of an <b>electric</b> lamp, which gives out light when <b>electricity</b> passes through it.
<b>buzzers</b>	An <b>electrical</b> device used to make a buzzing sound.
<b>circuit</b>	A complete route which an <b>electric current</b> can flow around.
<b>conductors</b>	A substance that heat or <b>electricity</b> can pass through or along.
<b>current</b>	A flow of <b>electricity</b> through a <b>wire</b> or <b>circuit</b> .
<b>electricity</b>	A form of energy that can be carried by <b>wires</b> and is used for hearing and lighting and to provide power for devices.
<b>insulator</b>	A non- <b>conductor</b> of electricity or heat.
<b>mains</b>	Where the supply of <b>electricity</b> enters a building.
<b>motor</b>	A device that uses <b>electricity</b> to produce movement.
<b>plug</b>	Makes an <b>electrical</b> connection between an <b>appliance</b> and the <b>mains</b> .
<b>source</b>	Where something comes from
<b>switch</b>	A small control for an <b>electrical</b> device which you use to turn the device on or off
<b>wire</b>	A long thin piece of metal that is used to fasten things or carry <b>electric current</b> .